

CENG3420

Lab 3-2: RISC-V-LC Datapath

Chen BAI

Department of Computer Science and Engineering
The Chinese University of Hong Kong

ybai@cse.cuhk.edu.hk

Spring 2021



香港中文大學

The Chinese University of Hong Kong

Overview

Background

Introduction

Lab3-2 Assignment



Overview


Background

Introduction


Lab3-2 Assignment




Datapath

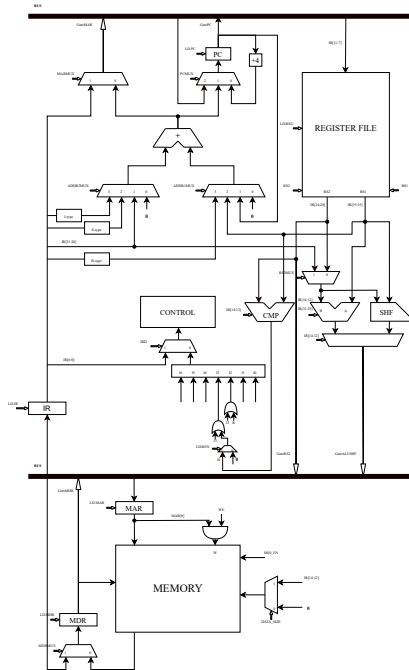

Datapath Annotation

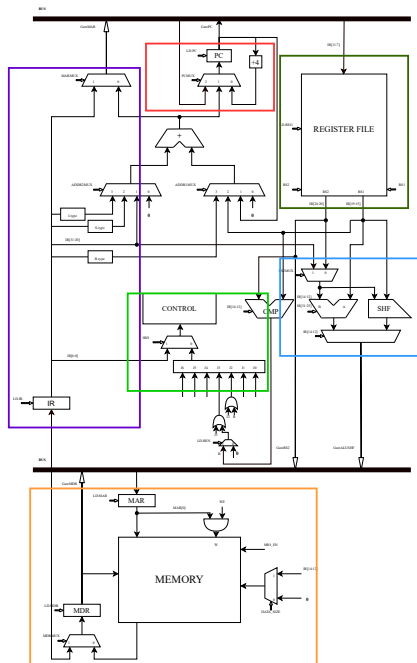

Datapath Annotation

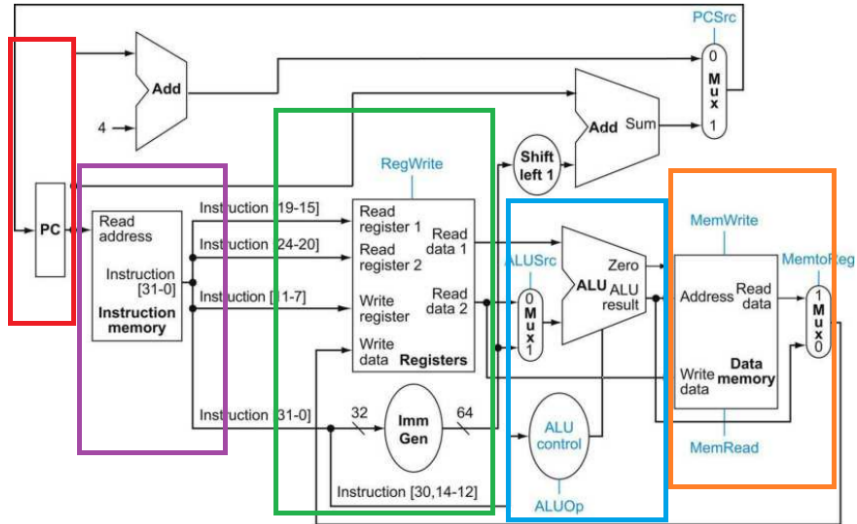


RISC-V datapath annotation based on the textbook



FSM

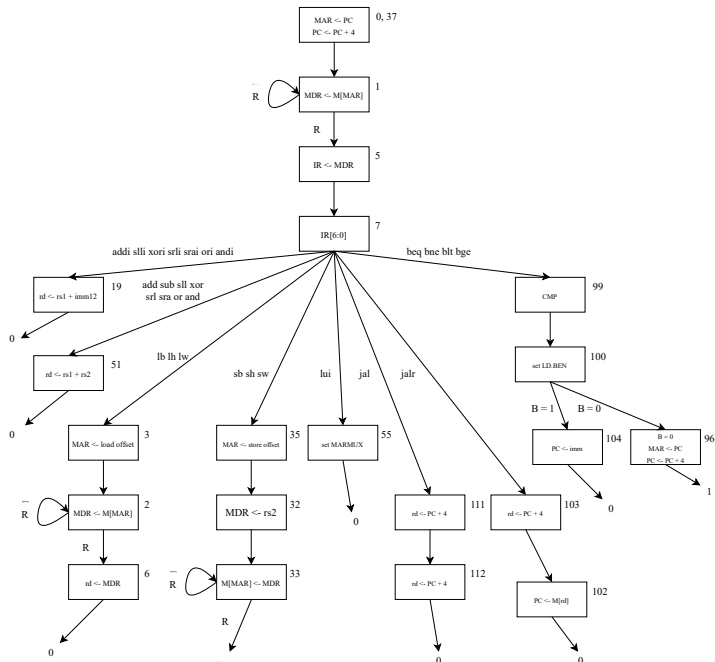- ▶ Clock cycle: The cycle time of a microprocessor is the duration of a clock cycle
- ▶ Finite State Machine: The behavior of the RISC-V-LC microarchitecture during a given clock cycle is completely determined by the 33 control signals. These 33 control signals specify the state of the control structure of the RISC-V-LC microarchitecture.





Overview

Background


Introduction

Lab3-2 Assignment



MUXs

You should pay attention to some MUXs

 

3-8 Decoder

■	A2,A1,A0	→	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
■	000	→	0	1	1	1	1	1	1	1
■	001	→	1	0	1	1	1	1	1	1
■	010	→	1	1	0	1	1	1	1	1
■	011	→	1	1	1	0	1	1	1	1
■	100	→	1	1	1	1	0	1	1	1
■	101	→	1	1	1	1	1	0	1	1
■	110	→	1	1	1	1	1	1	0	1
■	111	→	1	1	1	1	1	1	1	0

3-8 Decoder Truth Table



MUXs

- ▶ blockDATASIZEMUX: related to DATA_SIZE, i.e., sb/sh/sw/lb/lh/lw (IR[14:12], 0)
- ▶ blockADDR2MUX (0, SEXT(IR[31:20]) SEXT(S-type), SEXT(J-type))
- ▶ blockADDR1MUX (0, PC, IR[19:15], SEXT(B-type))
- ▶ blockMARMUX (valueOfMARMUXFromAdder, IR[31: 12] \ll 20)
- ▶ blockRS2MUX (REGS[IR[24, 20]], sext(IR[31:20]))
- ▶ blockALUSHFMUX (valueOfALU, valueOfSHF)
- ▶ blockMDRMUX (MemOut, BUS)
- ▶ blockPCMUX (PC + 4, BUS)



Tristate Drivers

You should pay attention to BUS values, and it can be

- ▶ 0
- ▶ valueOfGateMAR
- ▶ valueOfGateALUSHF
- ▶ valueOfGatePC
- ▶ valueOfGateRS2
- ▶ valueOfGateMDR

How do we assign BUS with these value?

0 - BUS = 0

1 - BUS = valueOfGateMAR

2 - BUS = valueOfGateALUSHF

4 - BUS = valueOfGatePC

8 - BUS = valueOfGateRS2

16 - BUS = valueOfGateMDR



Overview

Background

Introduction

Lab3-2 Assignment



Lab3.2 Assignment

It is challenging! In fact, there is still a plenty of optimization opportunities for the current system.

RISCV-LC codes have been released on [22 Apr.](#)

- ▶ `git clone https://github.com/baichen318/ceng3420.git; cd ceng3420`
- ▶ `git checkout lab3.2`

Compile (Linux + x86_64 environment is suggested)

- ▶ `make`

Run RISCV-LC

- ▶ `./lc uop benchmarks/isa.bin # RISCV-LC runs isa.bin`



Lab3.2 Assignment

- ▶ Finish `cycle_memory`
- ▶ Finish `eval_bus_drivers`
- ▶ Finish `drive_bus`
- ▶ Finish `latch_datapath_values`

These unimplemented codes are annotated with [Lab3-2 assignment](#)



Lab3.2 Assignment

Verify your codes with binary machine codes suffixed with .bin

- ▶ isa.bin
- ▶ count10.bin
- ▶ swap.bin

Submission Method:

Prepare a package into [blackboard](#), including

- ▶ All source codes (C source files, header files, Makefile, etc.)
- ▶ A lab report (<name-sid>-lab3.pdf) with **all console results** and **some illustrations of your implementation**.
- ▶ Deadline: **23:59, 11 May**



Thanks. For any question:
byu@cse.cuhk.edu.hk
cbai@cse.cuhk.edu.hk
ybai@cse.cuhk.edu.hk

