
CENG4480 Homework 2

Due: Nov. 13, 2018

- Q1 The circuit shown in Figure 1 represents a simple 4-bit digital-to-analog converter. Each switch is controlled by the corresponding bit of the digital number if the bit is 1 the switch is up; if the bit is 0 the switch is down. Let the digital number be represented by $b_3b_2b_1b_0$. Please answer the following two questions:
 - (1) Determine an expression relating v_o to the binary input bits.
 - (2) Use this converter, design another 4-bit digital-to-analog converter whose output is given by

$$v_o = -\frac{1}{10}(8b_3 + 4b_2 + 2b_1 + b_0)V. \tag{1}$$

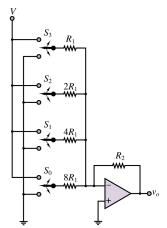

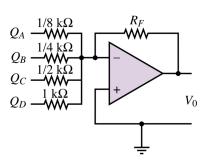


Figure 2: RF DAC.

Figure 1: 4-bit DAC.

- **Q2** For the DAC circuit shown in Figure 2 (using an ideal op-amp), what value of R_F will give no utput range of $-10 \le V_0 \le 0V$? Assume that logic 0 = 0V and logic 1 = 5V.
- **Q3** A simple Infra-Red Sensor system to detect passing human is presented as in Figure 3. A and B are IR Sensors which will generate different output voltages for different infra-red intensity, and higher voltage level corresponds to high light intensity.
 - (1) Explain how this system works for counting passing pedestrians.
 - (2) To increase counting accuracy, usually B is covered with materials that can reflect infra-red light. Explain why.



Figure 3: IR-System.

- **Q4** Exemplify the working principles of sensors that measure: (1) Flow; (2) Temperature; (3) Pressure; (4) Motion; (5) Liquid Level.
- **Q5** Briefly describe how PID affects motor control.
- Q6 Given a linear system

$$\begin{cases} x_t = A_{t-1}x_{t-1} + \omega_{t-1}, \\ z_t = B_tx_t + v_t, \\ v_t = C_{t-1}v_{t-1} + n_{t-1}, \end{cases}$$
(2)

where ω_t and n_t are independent and obey Gaussian distribution zero-mean and covariance Q_t and R_t , respectively. Please give the estimate equation and measurement equation of the system.

- **Q7** Given two Gaussian distributions $N\left(x_0; \mu_0, \sigma_0\right)$ and $N\left(x_1; \mu_1, \sigma_1\right)$, try to give the expectation and variance of a new distribution which is the product of these two Gaussian distributions.
- **Q8** For the 4-bit R-2R DAC, calculate V_0 in terms of $V_{b,0} V_{b,4}$ if V_{ref} is grounded (Figure 4).

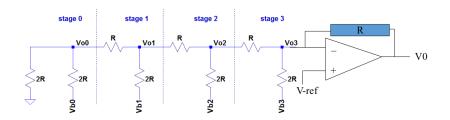


Figure 4: R-2R DAC.

Q9 [UPDATED] Assume the liner estimate system equation is $\mathbf{x}_{t+1} = \mathbf{A}\mathbf{x}_t + \mathbf{w}_t$. Given a second-autoregression random series:

$$x(t) = 2.32x(t-1) - 0.76x(t-2) + \omega_t \tag{3}$$

Kalman Filter is used to estimate x(t) (Here x(t) is a scalar). Try to give the formulations of state transition matrix \mathbf{A} and noise vector \mathbf{w}_t .