

CENG4480 Homework 3

Q-1 Given

- $T_{ff} = 8ns;$
- $TG = 6ns;$
- $T_{setup} = 4ns;$
- $T_{CLK} = 40MHz;$

What's the biggest time skew allowed?

Q-2 Given the logic circuit as shown in Figure 1, please write down outputs s and c_{out} w. r. t. inputs a, b and c . What the function of this circuit?

 


Figure 1: The Logic Circuit for Question 3

Q-3 Analysis the properties of SRAM, DRAM, SDRAM and DDR-SDRAM.

Q-4 What is the modern memory hierarchy? Plz draw the figure and Analyze the corresponding properties of each hierarchy level.


Q-5 The general equation of a liner estimate system is like $\mathbf{x}_{t+1} = \mathbf{A}\mathbf{x}_t + \mathbf{w}_{t+1}$. Given a second-autoregression random series:

$$x(t) = 2.32x(t - 1) - 0.76x(t - 2) + \omega_t \quad (1)$$

Kalman Filter is used to estimate $x(t)$ (Here $x(t)$ is a scalar). Try to give the formulations of state transition matrix \mathbf{A} and noise vector \mathbf{w}_t .

Q-6 A digital clock is important in circuit design. Please answer the following **three** questions.

 (a) Given the following circuit, $CLK1 = CLK2 = 25MHz$; $T_{ff} = 5ns$; $T_{setup} = 5ns$. The gate delay $TG = 10ns$. Please calculate the time margin. Note: T_{ff} = delay of a flip flop, T_{setup} =setup time of a flip flop, and TG is delay of a gate.



(b) In the above circuit, currently there is already one delay gate with delay TG . How many more similar delay gates can you insert between A and B without creating error?

(c) Sometimes we can take advantage of clock skew. For the above circuit, if the delay from CLK to $CLK2$ is $4ns$, calculate the minimal clock period of the clock CLK .

Q-7 Given the 6T-SRAM cell as in Figure 2, discuss the reading behavior (i.e., reading steps) if originally $A = 1$, $A_b = 0$.

 


Figure 2: 6T-SRAM cell structure.