

CENG 4480

Embedded System Development & Applications



Lecture 03: Operational Amplifier – 2

Bei Yu

CSE Department, CUHK

byu@cse.cuhk.edu.hk

(Latest update: October 27, 2021)

Fall 2021



- ① Preliminaries
- ② Integrator & Differentiator
- ③ Filters



- 1 Preliminaries
- 2 Integrator & Differentiator
- 3 Filters



$$e^{j\theta} = \cos\theta + j\sin\theta$$

- real component
- imaginary component
- magnitude

$$|e^{j\theta}| = \sqrt{\cos^2\theta + \sin^2\theta} = 1$$




Prove:

$$\left| \frac{1}{1 + ja} \right| = \frac{1}{\sqrt{1 + a^2}}$$



$$x(t) = A\cos(\omega t + \phi)$$

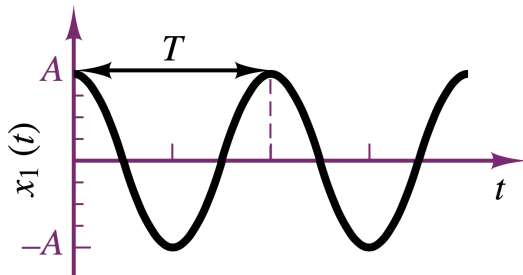- Periodic signals
- A : amplitude
- ω : radian frequency
- ϕ : phase






- Voltage gain against time

For sinusoidal signal:

$$v(t) = A\cos(\omega t + \phi)$$

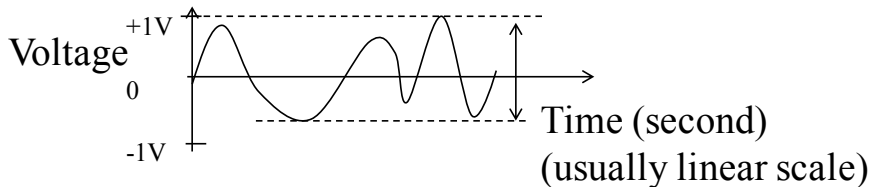





- Voltage gain against frequency

For sinusoidal signal:
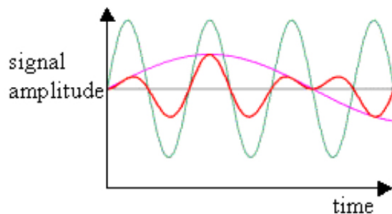
$$\mathbf{V}(j\omega) = Ae^{j\phi} = A\angle\phi = A\cos\phi + jA\sin\phi$$



Time domain

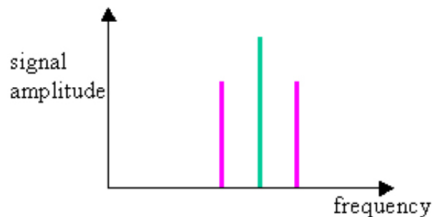


Frequency domain



Impedance

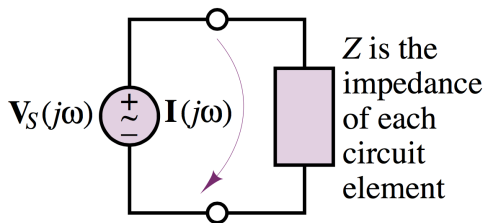A complex resistance or *frequency-dependent resistance*. That is, as resistors whose resistance is a function of the frequency of the sinusoidal excitation.




AC circuits in
phasor/impedance form




Assume source voltage $v = A \cos(\omega t)$, then

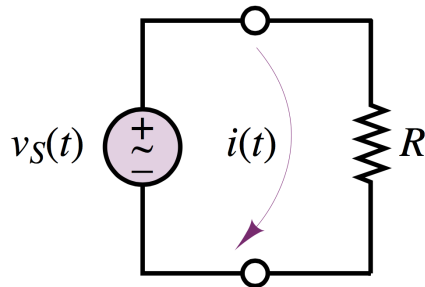- $\mathbf{V}(j\omega) = A\angle 0$
- $\mathbf{I}(j\omega) = \frac{A}{R}\angle 0$




Impedance of A Resistor
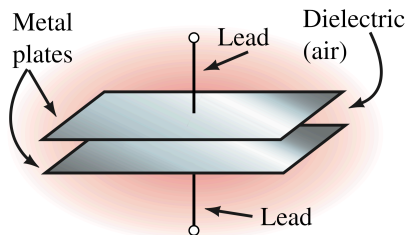
$$Z_R(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)} = R\angle 0 = R$$



(a) Basic construction

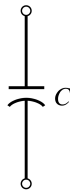

(b) Symbol

Capacitance C


A measure of how much charge a capacitor can hold.

- Amount of charge $Q = C \cdot V$

- **current** is the rate of movement of charge: $I = \frac{dQ}{dt} = C \cdot \frac{dV}{dt}$


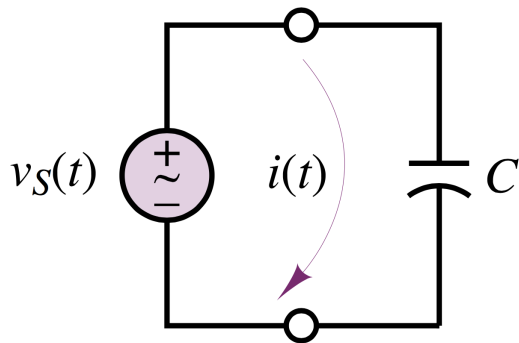
$$\mathbf{V}(j\omega) = A\angle 0$$
$$\mathbf{I}(j\omega) = \omega CA\angle \pi/2$$




Impedance of A Capacitor

$$Z_C(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)}$$


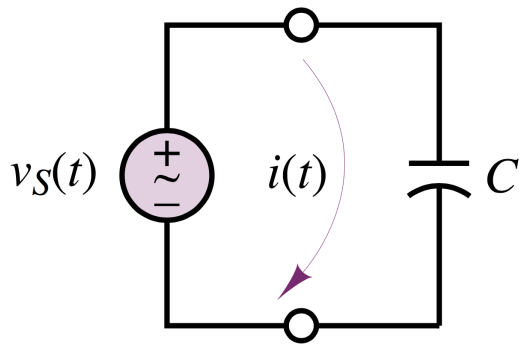
$$\mathbf{V}(j\omega) = A\angle 0$$
$$\mathbf{I}(j\omega) = \omega CA\angle \pi/2$$




Impedance of A Capacitor

$$Z_C(j\omega) = \frac{\mathbf{V}(j\omega)}{\mathbf{I}(j\omega)}$$



$$Z_C(j\omega) = \frac{1}{j\omega C}$$

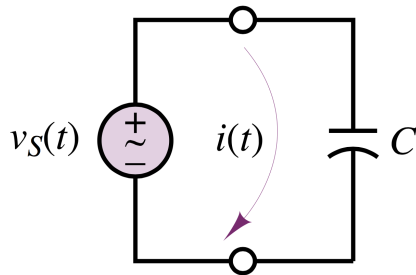

Capacitor Rule 1

Low Frequency \Rightarrow Open circuit


Capacitor Rule 2

High Frequency \Rightarrow Short circuit




- 1 Preliminaries
- 2 Integrator & Differentiator
- 3 Filters


Frequency Response of An Op-Amp

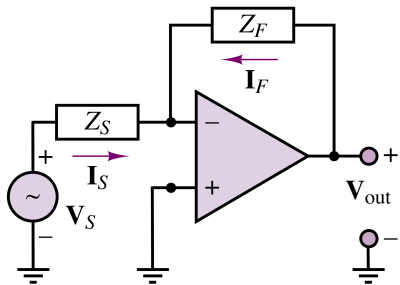


Inverting

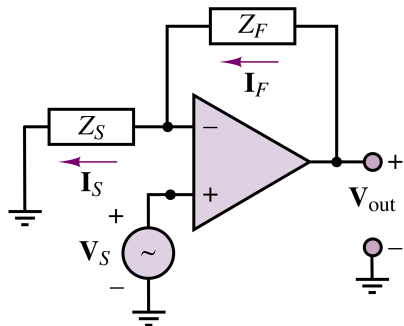

Noninverting

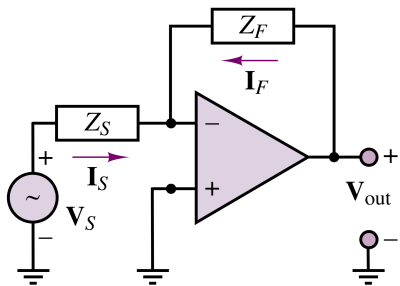


Inverting

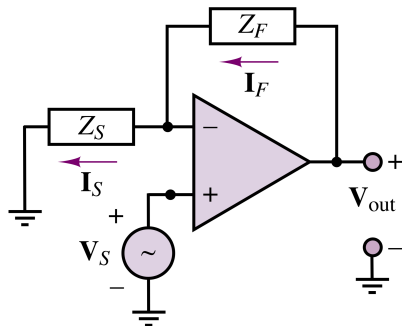


Noninverting

- Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = -\frac{Z_F}{Z_S}$

Frequency Response of An Op-Amp

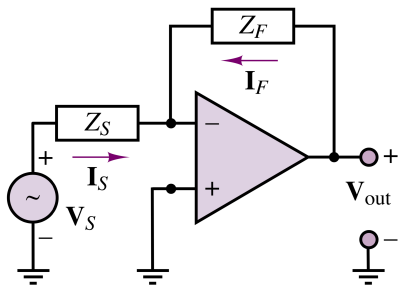


Inverting

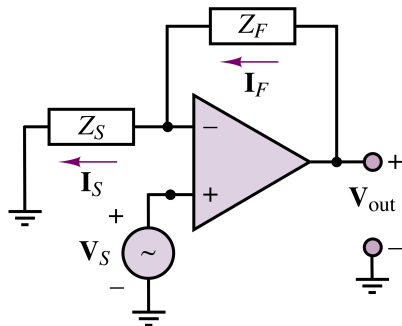

Noninverting

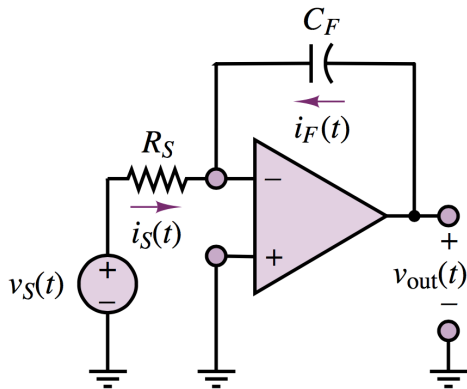
- Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = -\frac{Z_F}{Z_S}$
- Non-Inverting amplifier: $\frac{V_{out}}{V_S}(j\omega) = 1 + \frac{Z_F}{Z_S}$



$$i_S(t) = -i_F(t)$$

$$i_S(t) = \frac{v_S(t)}{R_S}$$
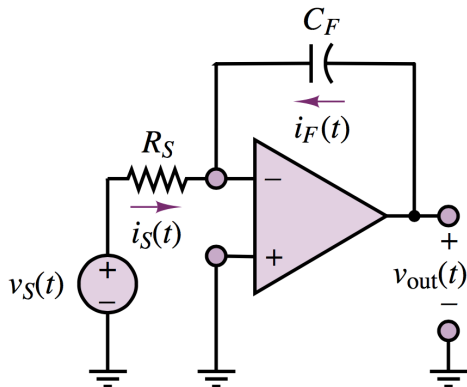
$$i_F(t) = C_F \cdot \frac{dv_{out}(t)}{dt}$$




$$i_S(t) = -i_F(t)$$

$$i_S(t) = \frac{v_S(t)}{R_S}$$

$$i_F(t) = C_F \cdot \frac{dv_{out}(t)}{dt}$$


Therefore:
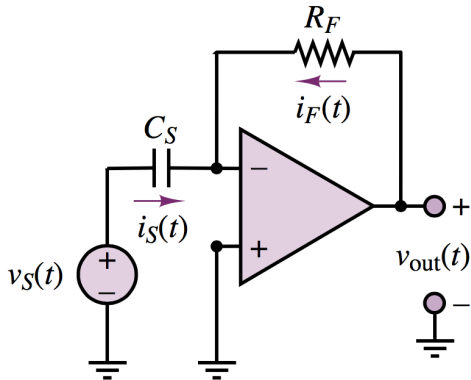
$$v_{out}(t) = -\frac{1}{R_S C_F} \int_{-\infty}^t v_S(t') dt'$$



$$i_S(t) = C_S \cdot \frac{dv_S(t)}{dt}$$

$$i_F(t) = \frac{v_{out}(t)}{R_F}$$

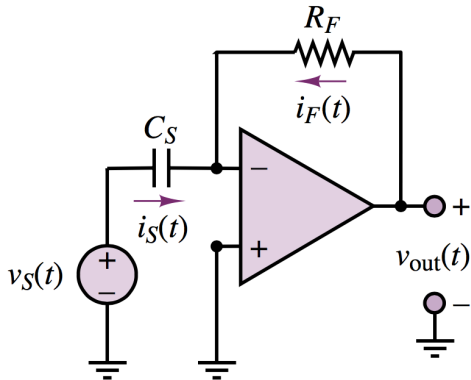

$$i_S(t) = C_S \cdot \frac{dv_S(t)}{dt}$$


$$i_F(t) = \frac{v_{out}(t)}{R_F}$$

Therefore:

$$v_{out}(t) = -R_F C_S \cdot \frac{dv_S(t)}{dt}$$



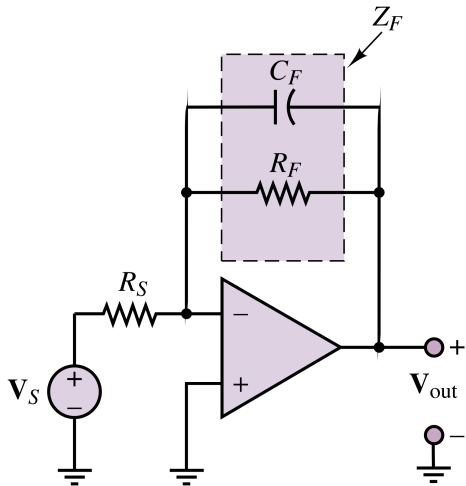
- 1 Preliminaries
- 2 Integrator & Differentiator
- 3 Filters



$$A(j\omega) = -\frac{Z_F}{Z_S}$$

$$Z_F = R_F \parallel \frac{1}{j\omega C_F} = \frac{R_F}{1 + j\omega C_F R_F}$$

$$Z_S = R_S$$

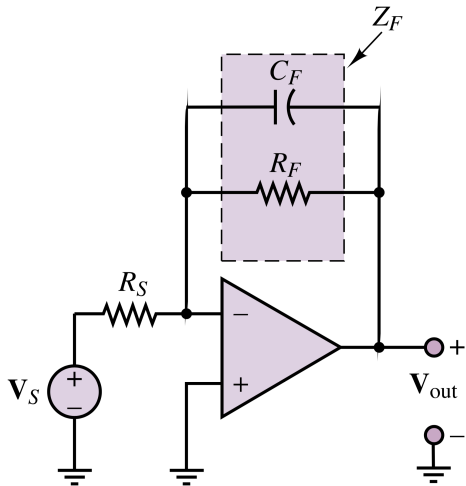

$$A(j\omega) = -\frac{Z_F}{Z_S}$$

$$Z_F = R_F \parallel \frac{1}{j\omega C_F} = \frac{R_F}{1 + j\omega C_F R_F}$$

$$Z_S = R_S$$

⇒

$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{R_F/R_S}{1 + j\omega C_F R_F}$$




Given:


$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{R_F/R_S}{1 + j\omega C_F R_F}$$
$$\omega_c = \frac{1}{R_F C_F}$$

Prove:

$$|A| = \frac{R_F}{R_S} \cdot \frac{1}{\sqrt{1 + \omega^2/\omega_c^2}}$$

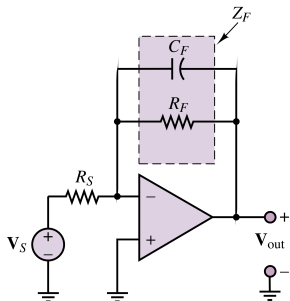

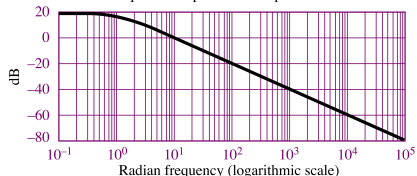
dB amplitude response of low-pass active filter



$$|A| = \frac{R_F}{R_S} \cdot \frac{1}{\sqrt{1 + \omega^2/\omega_c^2}}$$

- $\omega_c = \frac{1}{R_F C_F}$
- **3-dB** frequency
- or **cutoff** frequency

BTW, $\lim_{\omega \rightarrow 0} |A| = \frac{R_F}{R_S}$, $\lim_{\omega \rightarrow \infty} |A| = 0$

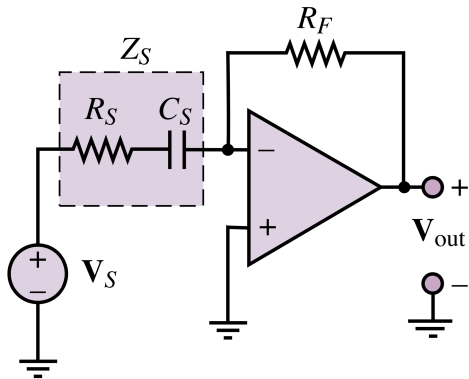

$$A(j\omega) = -\frac{Z_F}{Z_S}$$



$$Z_S = R_S + \frac{1}{j\omega C_S}$$

$$Z_F = R_F$$

⇒

$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{j\omega C_S R_F}{1 + j\omega C_S R_S}$$

High-Pass Filter

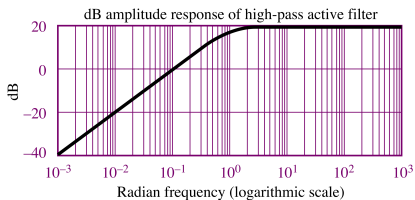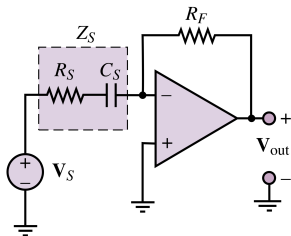

$$A(j\omega) = -\frac{Z_F}{Z_S} = -\frac{j\omega C_S R_F}{1 + j\omega C_S R_S}$$

$$\lim_{\omega \rightarrow 0} |A| = 0$$

$$\lim_{\omega \rightarrow \infty} |A| = \frac{R_F}{R_C}$$

High freq. cutoff unintentionally created by Op-amp

