

# CENG 4480

## Embedded System Development & Applications



### Lecture 11: Clock

Bei Yu

CSE Department, CUHK

[byu@cse.cuhk.edu.hk](mailto:byu@cse.cuhk.edu.hk)

(Latest update: October 27, 2021)

Fall 2021




# Clock Timing
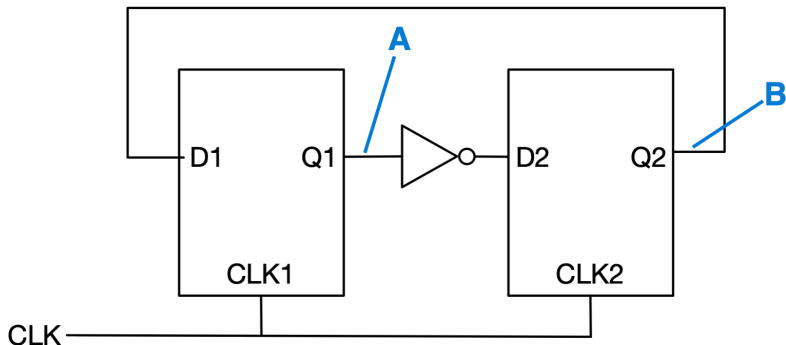
# A 2-bit ring counter example




- 2-bit ring counter
- Initially  $A = B = 0$ ;  $A = 0011001100$
- What is  $B$ ?


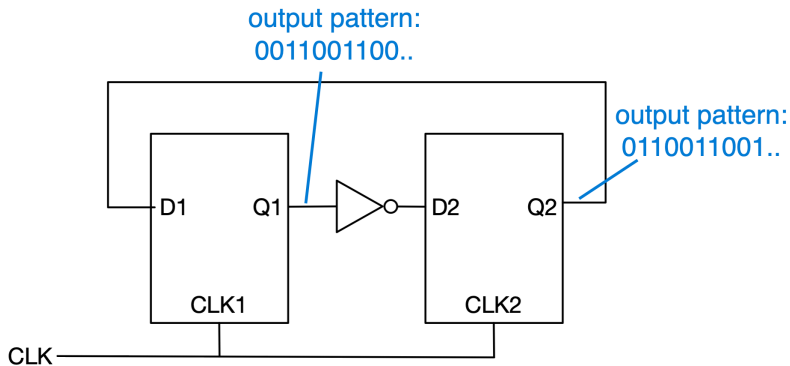
# A 2-bit ring counter example



- The result is Okay when clock is slow
- But, when clock is TOO fast, get some problem







- **Setup Time:** The time that the input data must be stable before the clock transition of the system occurs
- **Time Margin:** measures the slack, or excess time, remaining in each clock cycle
  - Protects your circuit against signal cross-talk, miscalculation of logic delays, and later minor changes in the layout
  - Depends on both time delay of logic paths and clock interval



 - $T_{ff}$ : delay of flip-flop (FF)
- $T_G$ : delay of gate G, including track delay
- $T_{setup}$ : worst-case setup time required by FF2, data at D2 must arrive at least  $T_{setup}$  before  $CLK_2$


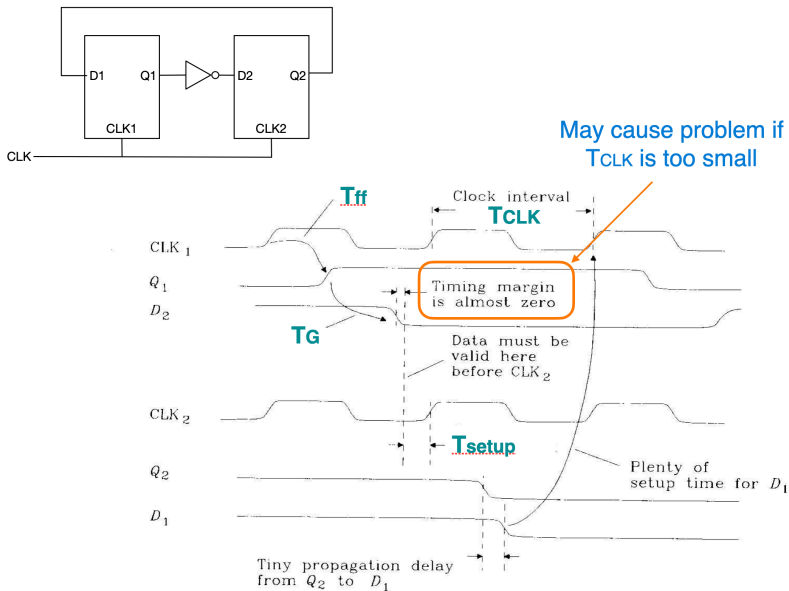
# May cause problem if $T_{CLK}$ is too small





 
## EX. B2-1

$CLK1 = CLK2 = 20MHz$ ;  $T_{ff} = 8ns$ ;  $T_{setup} = 5ns$ ;  $TG = 10ns$ .

- Find time margin
- How many delay G gates can you insert between A and B without creating error?








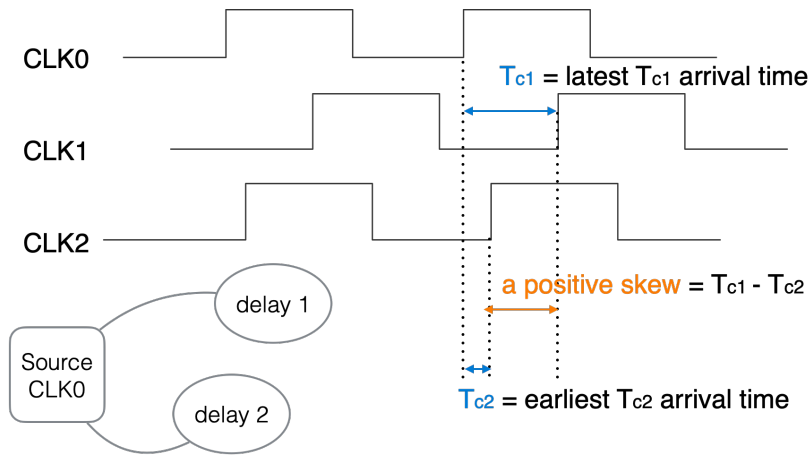
# Clock Skew



- The clock does NOT reach FF1, FF2 at the same time




# Why Care Clock Skew?

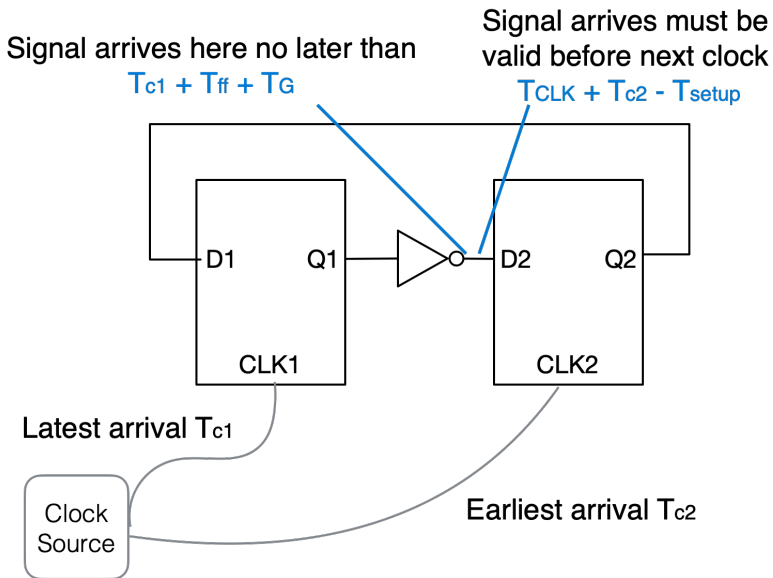



 - $T_{delay} = T_{c1} + T_{ff} + T_G$
- $T_{clk'} = T_{CLK} + T_{c2} - T_{setup}$
- Since  $T_{delay} < T_{clk'} \Rightarrow$





## EX. B2-2

Given

- $T_{ff} = 7\text{ns};$
- $T_G = 5\text{ns};$
- $T_{setup} = 4\text{ns};$
- $T_{CLK} = 40\text{MHZ};$


What's the biggest time skew allowed?


**Answer:**




- Drive them from the same source & balance the delays
- **Style 1:** Spider-leg distribution network
  - use a power driver to drive N outputs.
  - Use load (R) termination to reduce reflection if the traces are long (distributed circuit). Total load =  $R/N$ .
  - Two or more driver outputs in parallel may be needed.
- **Style 2:** Clock distribution tree


# Style 1: Spider-leg Clock

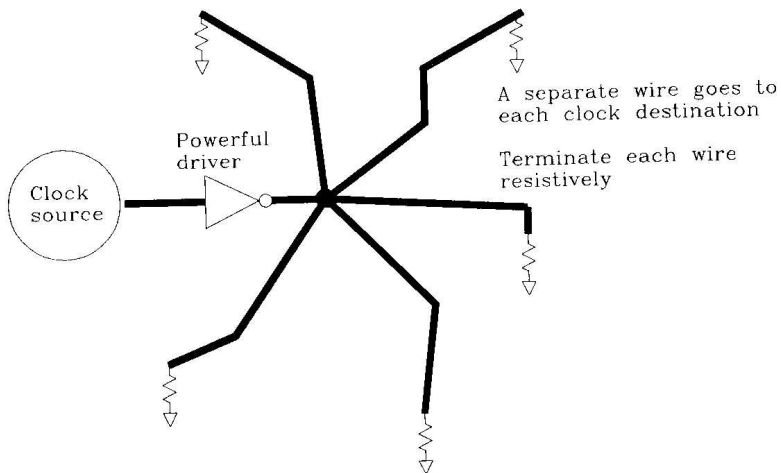


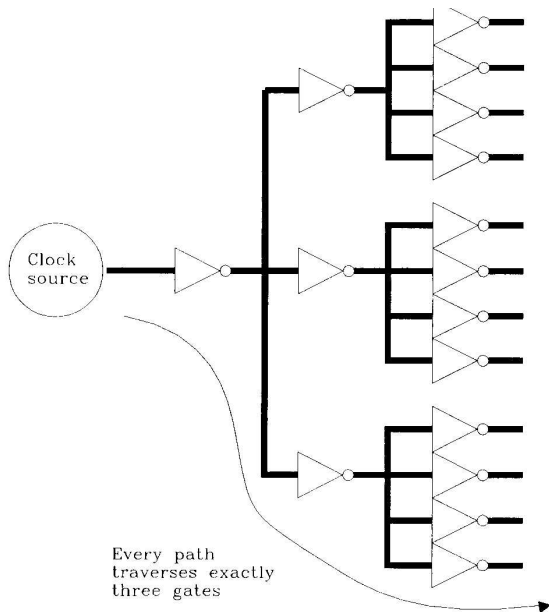




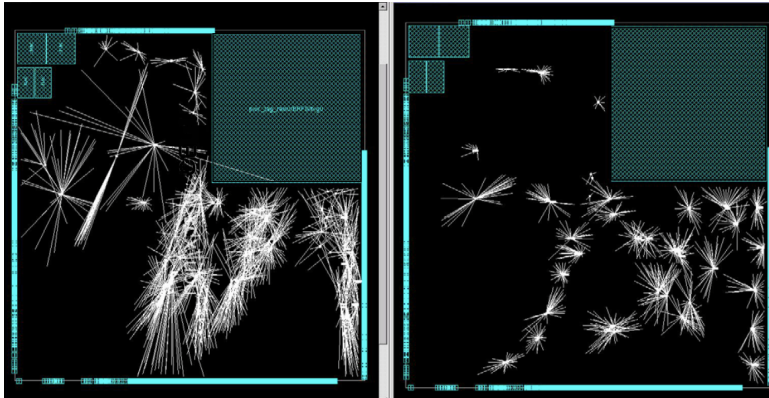

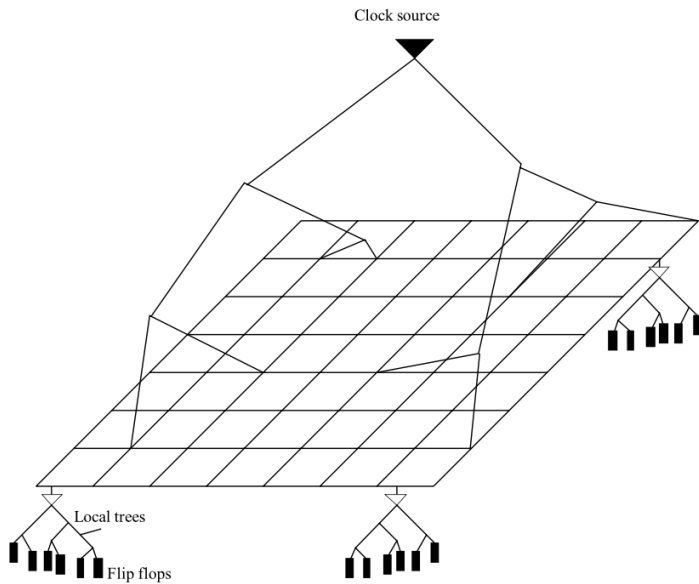

 

 




# Skew Optimization



Instead of Zero-Skew, take advantage of Skew.

 Question:

Given  $T_G=6\text{ns}$ ,  $T_{ff}=10\text{ns}$ ,  $T_{setup}=2\text{ns}$ , what's the minimal  $T_{CLK}$ ? Assume  $T_{c3} = 0$ .





**Thank You**