



香港中文大學

The Chinese University of Hong Kong

CENG3430 Rapid Prototyping of Digital Systems

Lecture 08:

Use of Signals and Variables

Ming-Chang YANG

mcyang@cse.cuhk.edu.hk






- Revisit: Signal (\leftarrow) and Variable ($:=$) Assignments
- Use of Signals and Variables
 - Outside Process: Concurrent Statement
 - Inside Process: Sequential Statement
 - Combinational Process
 - Sequential Process

Revisit: Signal Assignment (<=)



 
- **Signal Assignment (<=)**
 - Global to the **entity**
 - **Concurrent** execution
 - Do not be confused with the operator <= (equal or smaller)
- For example: **A1 <= B1 or C1**
 - A1 must be declared outside a process.
 - A1 represents an **internal wire** or an **input/output pin in port**.



Revisit: Variable Assignment ($:=$)



 - **Variable Assignment ($:=$)**
 - Local to a **process**
 - Sequential execution
 - Constant/signal/variable initialization also uses “ $:=$ ”
- For example: **$A2 := B2 \text{ or } C2$**
 - $A2$ must be declared inside a process.
 - $A2$ must be a **variable**.



Overview: Use of Signals and Variables

architecture body

Outside Process

process (sensitivity list)

Combinational Process

NO Clock Triggering

if/wait until CLK;

Sequential Process

Clock Triggering Exists

1) Synchronous Inputs

NOT in sensitivity list

2) Asynchronous Inputs

IN sensitivity list

- **Outside Process**
 - Concurrent Statements
- **Inside Process**
 - Sequential Statements
 - 1) **Combinational Process:**
NO **CLK** triggering
 - “<=” is a combinational logic
 - All involved inputs should be in the sensitivity list
 - 2) **Sequential Process:**
Has **CLK** triggering
 - “<=” is a flip-flop
 - **Synchronous Inputs:** should NOT be in the sensitivity list
 - **Asynchronous Inputs:** should be in sensitivity list

Overview: Use of Signals and Variables

architecture body

Outside Process

process (sensitivity list)

Combinational Process

NO Clock Triggering

if/wait until CLK;

Sequential Process

Clock Triggering Exists

1) Synchronous Inputs

NOT in sensitivity list

2) Asynchronous Inputs

IN sensitivity list

- **Outside Process**

- Concurrent Statements

- **Inside Process**

- Sequential Statements

- 1) **Combinational Process:**
NO CLK triggering

- “<=” is a combinational logic
- All involved inputs should be in the sensitivity list

- 2) **Sequential Process:**
Has CLK triggering

- “<=” is a flip-flop
- **Synchronous Inputs:** should NOT be in the sensitivity list
- **Asynchronous Inputs:** should be in sensitivity list

Outside Process: Concurrent Statement

- **Signal Assignments** **outside a Process**

- All the statements outside processes are “concurrent”.
 - All concurrent statements can be **interchanged** freely.
 - Each statement will be **executed once** when any signal in it changes.
- Signals can be assigned with **multiple values** if “**resolved logic**” (i.e., `std_logic` rather than `std_u`logic) is allowed.

Ex: architecture `test_arch` of `test` is

```
    out1 <= in1 and in2;  -- concurrent statement
    out2 <= in1 or in2;  -- concurrent statement
    out2 <= in2;         -- multi-value assignment
end test_arch;
```

- **Variable Assignments** **outside a Process**

- Variables can only live **inside** processes!



Overview: Use of Signals and Variables

architecture body

Outside Process

process (sensitivity list)

Combinational Process

NO Clock Triggering

if/wait until CLK;

Sequential Process

Clock Triggering Exists

1) Synchronous Inputs

NOT in sensitivity list

2) Asynchronous Inputs

IN sensitivity list

- **Outside Process**
 - Concurrent Statements
- **Inside Process**
 - Sequential Statements
 - 1) **Combinational Process:**
NO CLK triggering
 - “<=” is a combinational logic
 - All involved inputs should be in the sensitivity list
 - 2) **Sequential Process:**
Has CLK triggering
 - “<=” is a flip-flop
 - **Synchronous Inputs:** should NOT be in the sensitivity list
 - **Asynchronous Inputs:** should be in sensitivity list

Inside Process: Sequential Statement



- Statements inside **process** are executed **sequentially**.
 - The process will be **executed once** when one or more signals in the **sensitivity list** changes.

```
Ex: process (in1, in2) -- sensitivity list
      variable v1, v2: std_logic;
begin
    s1 <= in1 and in2;
    s1 <= in1 or in2;
    v1 := in1 and in2;
    v1 := in1 or in2;
end process
```

- **Signals Assignments (<=)** inside a Process:
Only the last assignment for a particular signal takes effect.
- **Variables Assignments (:=)** inside a Process:
All assignments take effect **immediately** and **sequentially**.

- A process can be: “**combinational**” or “**sequential**”.

Overview: Use of Signals and Variables

architecture body

Outside Process

process (sensitivity list)

Combinational Process

NO Clock Triggering

if/wait until CLK;

Sequential Process

Clock Triggering Exists

1) Synchronous Inputs

NOT in sensitivity list

2) Asynchronous Inputs

IN sensitivity list

- **Outside Process**
 - Concurrent Statements
- **Inside Process**
 - Sequential Statements
 - 1) Combinational Process:**
NO **CLK** triggering
 - “<=” is a combinational logic
 - All involved inputs should be in the sensitivity list
 - 2) Sequential Process:**
Has **CLK** triggering
 - “<=” is a flip-flop
 - **Synchronous Inputs:** should NOT be in the sensitivity list
 - **Asynchronous Inputs:** should be in sensitivity list

1) Combinational Process



- **Combinational Process**

- NO clock triggering condition can be found inside.
 - **Clock Triggering Condition:** `if (clk='1' and clk'event), (wait until clk='1'), etc.`
- Each “<=” is a **combinational logic**.
- All involved inputs should be in the **sensitivity list**.
 - Otherwise the results will be unpredictable.

```
Ex: combinational_process: process (in1, in2)
begin
    out3 <= in1 xor in2;
    out3 <= '1';
end process;
```

Class Exercise 8.1

Student ID: _____ Date: _____
Name: _____

```
1 signal S1, S2: bit;
2 signal S_OUT: bit_vector(1 to 8);
3 process (S1, S2)
4 variable V1, V2: bit;
5 begin
6   V1 := '1';
7   V2 := '1';
8   S1 <= '1';
9   S2 <= '1';
10  S_OUT(1) <= V1;
11  S_OUT(2) <= V2;
12  S_OUT(3) <= S1;
13  S_OUT(4) <= S2;
14  V1 := '0';
15  V2 := '0';
16  S2 <= '0';
17  S_OUT(5) <= V1;
18  S_OUT(6) <= V2;
19  S_OUT(7) <= S1;
20  S_OUT(8) <= S2;
21 end process;
```

- Which line(s) will NOT take effect?

Answer: _____

- When will the process be executed?

Answer: _____

- What are the values of **S_OUT** after execution?

Answer:

S_OUT(1) :	S_OUT(5) :
S_OUT(2) :	S_OUT(6) :
S_OUT(3) :	S_OUT(7) :
S_OUT(4) :	S_OUT(8) :

Overview: Use of Signals and Variables

architecture body

Outside Process

process (sensitivity list)

Combinational Process

NO Clock Triggering

if/wait until CLK;

Sequential Process

Clock Triggering Exists

- Outside Process
 - Concurrent Statements
- Inside Process
 - Sequential Statements
 - 1) **Combinational Process:**
NO CLK triggering
 - “<=” is a combinational logic
 - All involved inputs should be in the sensitivity list
 - 2) **Sequential Process:**
Has CLK triggering
 - “<=” is a flip-flop
 - **Synchronous Inputs:** should NOT be in the sensitivity list
 - **Asynchronous Inputs:** should be in sensitivity list

2) Sequential Process



- **Sequential Process (a.k.a. Clocked Process)**

- A **clock edge expression** can be found inside:

- **“if” statement:**

```
clocked_process: process (sensitivity list)
```

```
begin
```

```
... -- same as combinational process
```

```
if (clk='1' and clk'event) then
```

```
    out1 <= in1 and in2;
```

```
end if;
```

```
... -- same as combinational process
```

```
end process;
```

- **“wait until” statement:**

```
clocked_process: process -- no sensitivity list
```

```
begin
```

```
wait until clk='1';
```

```
    out1 <= in1 and in2;
```

```
end process;
```

1) Each “<=” is a **flip-flop**.

2) The assignment takes effect on next clock edge.

1) Each “<=” is a **flip-flop**.

2) The assignment takes effect on next clock edge.


Class Exercise 8.2

Student ID: _____ Date: _____

Name: _____

- Find the signal results after clock edges $t_1 \sim t_4$:
 
```
process
signal s1: integer:=1;
signal s2: integer:=2;
signal s3: integer:=3;
begin
wait until rising_edge(clk);
  s1 <= s2 + s3;
  s2 <= s1;
  s3 <= s2;
  sum <= s1 + s2 + s3;
end process
end
```



	t1	t2	t3	t4
s1				
s2				
s3				
sum				

Signals Assignments (\leftarrow) inside a Process:

Only *the last* assignment for a particular signal takes effect.

Variables Assignments ($:=$) inside a Process:

All assignments take effect **immediately** and **sequentially**.


Class Exercise 8.3

Student ID: _____ Date: _____

Name: _____

- Find the signal results after clock edges $t1 \sim t4$:
 
```
process
variable v1: integer:=1;
variable v2: integer:=2;
variable v3: integer:=3;
begin
wait until rising_edge(clk);
  v1 := v2 + v3;
  v2 := v1;
  v3 := v2;
  sum <= v1 + v2 + v3;
end process
end
```



	t1	t2	t3	t4
v1				
v2				
v3				
sum				

Signals Assignments (\leftarrow) inside a Process:

Only *the last* assignment for a particular signal takes effect.

Variables Assignments ($:=$) inside a Process:


All assignments take effect **immediately** and **sequentially**.

Do Variables Have Memory?



- **Yes.** After a process is called, the state of a variable will be kept for being used again next time.
 
```
library IEEE;
use IEEE.std_logic_1164.all;
entity test is port (a, reset_v1: in std_logic;
                    b, c: out std_logic); end test;
architecture test_arch of test is
begin
label_procl: process (a, reset_v1)
variable v1 : std_logic;
begin
    if reset_v1 = '1' then
        v1 := not a;
    end if;
    b <= a;
    c <= v1;
end process label_procl;
end test_arch;
```



v1 stays at two different levels depending on previous result.

Overview: Use of Signals and Variables

architecture body

Outside Process

process (sensitivity list)

Combinational Process

NO Clock Triggering

if/wait until CLK;

Sequential Process

Clock Triggering Exists

1) Synchronous Inputs

NOT in sensitivity list

2) Asynchronous Inputs

IN sensitivity list

- **Outside Process**
 - Concurrent Statements
- **Inside Process**
 - Sequential Statements
 - 1) **Combinational Process:**
NO CLK triggering
 - “<=” is a combinational logic
 - All involved inputs should be in the sensitivity list
 - 2) **Sequential Process:**
Has CLK triggering
 - “<=” is a flip-flop
 - **Synchronous Inputs:** should NOT be in the sensitivity list
 - **Asynchronous Inputs:** should be in sensitivity list


Synchronous & Asynchronous Inputs



- Besides of the clock signal (**CLK**), other signals in a **clocked process** can be classified into two types:
 - Synchronous Inputs** (e.g., **D** input of flip-flops)
 - Inputs that should be **checked** only at the next clock edge.
 - NO need to put synchronous input signals in the **sensitivity list**.
 - Asynchronous Inputs** (e.g., **RESET** input of flip-flops)
 - Inputs that should be **checked** either at the next clock edge or when any asynchronous input in the sensitivity list changes.
 - Asynchronous inputs **NEVER** exist in **wait-until** clocked processes.

```
process (CLK, RESET) -- no need to put D, why?
```
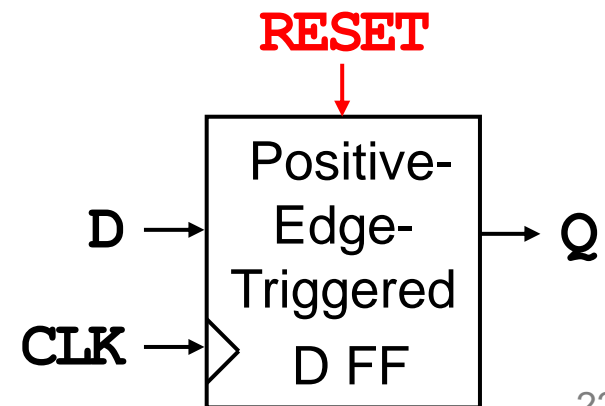
```
begin  
  if (RESET = '1') then  
    Q <= '0'; -- Reset Q immediately  
  elsif CLK = '1' and CLK'event then  
    Q <= D; -- Q follows input D  
  end if;  
end process;
```



Class Exercise 8.4

Student ID: _____ Date: _____
Name: _____

- What are processes p1 and p2 (combinational or sequential)?
- Which signals are sync., async., or combinational inputs?

...

```
port (clock, reset: in std_logic;  
      t_light: out std_logic_vector (2 downto 0));
```

...

```
type traffic_state_type is (s0, s1, s2, s3);  
signal t_state: traffic_state_type; -- internal signal  
p1: process(t_state)                p2: process  
begin                                begin  
  case (t_state) is                 wait until clock='1';  
    when s0 => t_light <= "100";    if reset = '1' then  
    when s1 => t_light <= "110";    t_state <= s0;  
    when s2 => t_light <= "001";    else  
    when s3 => t_light <= "010";    case t_state is  
  end case;                          when s0 => t_state <= s1;  
end process;                          when s1 => t_state <= s2;  
                                        when s2 => t_state <= s3;  
                                        when s3 => t_state <= s0;  
                                        end case;  
                                        end if;  
                                        end process;
```

Class Exercise 8.5

Student ID: _____ Date: _____
Name: _____

- Based on Class Exercise 7.4, rewrite process p2 using asynchronous reset.

```
sync_p2: process
begin
  wait until clock='1';
  if reset = '1' then
    t_state <= s0;
  else
    case t_state is
      when s0 => t_state <= s1;
      when s1 => t_state <= s2;
      when s2 => t_state <= s3;
      when s3 => t_state <= s0;
    end case;
  end if;
end process;
```

```
async_p2: process
begin
```

```
end process;
```

Recall: “wait until” vs. “if”

- **Asynchronous Process:** Computes values on clock edges or when asynchronous conditions are TRUE.
 - That is, it must be sensitive to the clock signal (if any), and to all inputs that may affect the asynchronous behavior.
 - **Rule:** Only use “**if**” for **asynchronous** process:

```
process (clk, input_a, input_b, ...)
begin
    ...
    if ( rising_edge (clk) )
    ...
end process
```

← The sensitivity list should include the clock signal, and all inputs that may affect asynchronous behavior.

Usage
of
“if”

Summary: Use of Signals and Variables

architecture body

Outside Process

process (sensitivity list)

Combinational Process

NO Clock Triggering

if/wait until CLK;

Sequential Process

Clock Triggering Exists

1) Synchronous Inputs

NOT in sensitivity list

2) Asynchronous Inputs

IN sensitivity list

- **Outside Process**
 - Concurrent Statements
- **Inside Process**
 - Sequential Statements
 - 1) **Combinational Process:**
NO **CLK** triggering
 - “<=” is a combinational logic
 - All involved inputs should be in the sensitivity list
 - 2) **Sequential Process:**
Has **CLK** triggering
 - “<=” is a flip-flop
 - **Synchronous Inputs:** should NOT be in the sensitivity list
 - **Asynchronous Inputs:** should be in sensitivity list

Summary: Inside Process



- **Signals Assignments (\leq) inside a Process**
 - Only the *last* assignment for a particular signal takes effect.
 - **Combinational Process:** No clock (CLK) triggering
 - Each “ \leq ” is a **combinational logic**.
 - All involved inputs should be in the **sensitivity list**.
 - **Sequential Process:** Has clock (CLK) triggering
 - Signal assignments *before* or *outside* the clock edge detection:
 - As the same as **combinational process (be careful!)**.
 - Signal assignments *after* or *inside* the clock edge detection:
 - Each “ \leq ” can be treated as a **flip-flop**: The signal assignment will take effect at the next clock edge.
 - **Synchronous inputs** should NOT be in the **sensitivity list**.
 - **Asynchronous inputs** should be in the **sensitivity list**.
- **Variables Assignments ($:=$) inside a Process**
 - All assignments take effect **immediately** and **sequentially**.

Summary: Multiple Assignments



- **Signals**

- **Outside Process**

- Signals can be assigned with multiple values (i.e., “multi-value” or “multi-driven”) **only if “resolved logic” is allowed.**
 - If not allowed? **Avoid assigning** a signal from multiple processes (or multiple concurrent statement).

- **Inside Process**

- Only the last assignment for that signal will take effect.

- **Variables**

- **Outside Process**

- Variables can only live inside processes!



- **Inside Process**

- ALL assignments take effect immediately and sequentially.