

CEG 5010: Rapid System Prototyping Section 3: VHDL Entities and Architectures

Philip Leong

"They know enough who know how to learn"
Henry Adams

A simple VHDL program (4 bit comparator), dataflow description

```
library ieee;
use ieee.std_logic_1164.all;
-- 4 bit comparator circuit
entity eqcomp4 is
    port (a, b: in std_logic_vector(3 downto 0);
          equals: out std_logic);    -- equals is active high
end eqcomp4;

architecture dataflow of eqcomp4 is
begin
    equals <= '1' when (a = b) else '0';
end dataflow;
```

Entities and Architectures

- Comments being with "--"
- Entity describes the I/O properties of the design
 - pinout/interface of the design
 - **in** means signal is an input (similarly **out** is an output)
 - `std_logic_vector` describes a 4 bit bus `a(0)`, `a(1)`, `a(2)`, `a(3)`
 - `std_logic_vector` is described as `(3 downto 0)` means 3 is the MSB
- Architecture describes its function
 - could be behavioural, structural or dataflow (more about this later)
 - "<=" is a signal assignment

Modes

- in - data only flows into the entity
- out - data only flows out of the entity
- buffer - an out signal that is used as in input to other parts of the cell
 - may not be driven by more than one output
 - can only connect to other buffer or an internal signals (not to out or inout signals)
- inout - for bidirectional signals (e.g. databus)
 - actually any signal can be replaced by inout but this is not encouraged for reasons of readability

Dataflow descriptions

- The assignment is a concurrent one
 - all assignments done in parallel (not sequentially like in a program)
 - ordering of the assignments does not matter

Behavioral description of eqcomp4

```
architecture behavioral of eqcomp4 is
begin
    comp: process(a, b)
    begin
        if (a = b) then
            equals <= '1';
        else
            equals <= '0';
        end if;
    end process comp;
end behavioral;
```

Behavioral description

- Can be synthesized
- algorithmic way of describing the circuit
- process is like a parallel task
- process statement includes a sensitivity list which describes which inputs are used in the process
 - when an input changes value, the process is executed
 - could also say (in this case ordering **does** matter)

```
equals <= '0';
if (a = b)
    equals <= '1';
end of;
```

Structural description of eqcomp4

architecture structural of eqcomp4 is

```
signal x : std_logic_vector(3 downto 0);
```

begin

```
u0: xnor2 port map (a(0), b(0), x(0));
```

```
u1: xnor2 port map (a(1), b(1), x(1));
```

```
u2: xnor2 port map (a(2), b(2), x(2));
```

```
u3: xnor2 port map (a(3), b(3), x(3));
```

```
u4: and4 port map (x(0), x(1), x(2), x(3), equals);
```

end structural;

Structural description

- Hierarchical netlist description
- Components instantiated and connected together with signals
- This description cumbersome and cannot be used if the number of bits changed

Behavioral, dataflow and structural descriptions for synthesizing circuits

- We can use all of these forms for synthesis
- normally easiest to
 - decompose circuit into small units
 - make behavioral or dataflow descriptions of blocks
 - simulate
 - connect together using structural
 - simulate
 - optimize by adding directives and/or changing descriptions

VHDL Synthesis

- VHDL is often used for simulation purposes only
 - like a programming language
 - only a subset is synthesizable
 - synthesized programs may not simulate in the expected way
- process statement execution
 - statements executed sequentially until last statement then waits for a change in one of the signals in the sensitivity list
 - although VHDL allows “wait” anywhere in the code, only makes sense in synthesis at the beginning or end of a process

Simulation, “wait” and “after”

```
proc1: process (a, b, c)
begin
    x <= a and b and c;
end process;
has same semantics as
proc2: process
begin
    x <= a and b and c;
    wait on a, b, c;
end process;
```

- the following works only in simulation (it doesn't make a lot of sense to synthesize such a circuit and synthesis software normally ignores “after”)

```
proc3: process (a, b, c)
begin
    x <= a and b and c after 5 ns;
end process;
```

- proc1 and proc2 makes the assignment one **delta delay** after a change in a, b or c in simulation


Incomplete sensitivity lists

```
proc5: process(a, b)
begin
  x <= a and b and c;
end process;
```

- note c not in sensitivity list
 - can we make a circuit that does proc5?
- synthesis software will either
 - say this is the same as proc1
 - give a warning/compile error

Simulation of VHDL

 - New values assigned δ time after the input changes
 - δ is an infinitesimally small value
 - to process concurrent statements, time only increased after all signals have been processed
 - “transition time” of logic
 - note we use digital logic in the same way
 - e.g. a and b are high for proc1



What happens in the following?

```
interesting: process(a, b, c)
begin
  x <= '0';
  if (a = b or c = '1') then
    x <= '1';
  end if;
end process interesting;
```

- if a, b, c are initially '0' and then c becomes '1' at 5 ns
 - 1st statement makes x=0 so it stays at this value up to 5ns
 - 3rd statement makes x=1 at 5+ δ ns

Execution model

1. all expressions on the RHS of a “<=” are computed
 - order does not matter
2. LHS updated at the end of a process statements to the **last assignment** of that variable *after a delay of δ*
 - NB δ is infinitely small

Another example

```
-- a, b, c initially zero
-- a goes high at 100ns
-- b goes high at 200ns

entity delta is port(
  a, b, c, d: in bit;
  u, v, w, x, y, z: buffer bit);
end delta;
```

```
architecture delta of delta is
begin
  z <= not y;
  y <= w or x;
  x <= u or v;
  v <= u and w;
  w <= c or d;
  u <= a and b;
end delta;
```

Why doesn't this work?

```
architecture xx of yy is
begin
  anding: process(a_bus)
  begin
    x <= '1';
    for i in 7 downto 0 loop
      x <= a_bus(i) and x;
    end loop;
  end process;
end xx;
```

- suppose initially a_bus is all 0's
- this always evaluates to x=0
 - a_bus(i) always 0 at time T so x always 0

Multiple drivers

- The following will cause a "multiple driver" error
architecture xx of yy is
begin
 y <= a and b;
 y <= a or b;
end xx;
- although obvious here, easy to do accidentally in different entities
- y <= a and b when oe = '1' else 'Z';

Adding don't care values

```
-- s is std_logic_vector
if s = "00" or s = "11" then
  y <= '1';
elsif s = "01" then
  y <= '0';
else
  y <= '-';
end if;
```

- '-' means 'don't care'
- in this case can make sure we generate
 - y = s1 + /s0;
- instead of
 - y = s1/s0+s1.s0

VHDL Identifiers

- Alphabetic, numerical and/or underscore
 - 1st character must be a letter
 - last character cannot be an underscore
 - 2 underscores in succession are not allowed
- upper and lower case are the same

Data Objects

- Constants
 - constant width: integer := 8;
- Signals
 - represent wires
 - signal count: std_logic_vector(3 downto 0);
 - initialized values ignored for synthesis but used in simulation
 - signal count: std_logic_vector(3 downto 0) := '1010';
 - ports are also signals
 - ports have modes
 - signals can be read or written

Data Objects (cont.)

- variables
 - used in functions and procedures
 - declared in the process or subprogram
 - do not represent wires
 - not well defined what they mean in terms of synthesis
 - we will avoid using them if possible since we aim to write portable VHDL code

Looped AND which does work using variables

```
architecture will_work of my_and is
begin
anding: process(a_bus)
  variable tmp: bit;
  begin
    tmp := '1';
    for i in 7 downto 0 loop
      tmp := a_bus(i) and tmp;
    end loop;
    x <= tmp;
  end process;
end will_work;
```

- := means an immediate assignment
 - recall <= scheduled after a delay of δ
- this now works like a C program would
 - tmp gets assigned straight away

Data objects

- Files
 - used for test benches (will discuss later)
- Aliases
 - an alternate identifier for an existing object
 - e.g. signal address: std_logic_vector(31 downto 0);
 - alias msb: std_logic_vector(7 downto 0) is address(31 downto 24);

Scalar Data types - enumeration

- enumeration
 - e.g.

```
type states is (idle, preamble,
data, jam, nofsd, error);
signal current_state: states;
```
 - these are ordered by the declaration
 - preamble < data
 - standard enumerations
 - type boolean is (FALSE, TRUE);
 - type bit is ('0', '1');
- type std_ulogic is
 - ('U', -- uninitialized
 - 'X', -- forcing unknown
 - '0', -- forcing 0
 - '1', -- forcing 1
 - 'Z', -- high impedance
 - 'W', -- weak unknown
 - 'L', -- weak 0
 - 'H', -- weak 1
 - '-', -- don't care
 - 'W', 'X', 'V' not supported by synthesis

Other Scalar Data Types

- Integer
 - 32 bit signed
 - signals or variables that are integers should be constrained to a range for synthesis
 - variable a: integer range -255 to 255;
- Floating point
 - only predefined is real
 - often not supported
- Time
 - type time is range -2147483647 to 2147483647 units fs;
 - fs, ps, ns, us, ms, sec, min, hr

Composite types - arrays

- Arrays
 - array bit_vector is array(natural range <>) of bit;
 - array std_logic_vector is array(natural range <>) of std_logic;
 - range <> means its not specified
 - can be any positive integer
 - you can define your own types
 - type word is array(15 downto 0) of std_logic;
 - signal w: word;
- two dimensional arrays
 - type table8x4 is array(0 to 7, 0 to 3) of bit;
 - constant exclusive_or: table8x4 := (

```
'000_0', '001_1',
'010_1', '011_0',
'100_1', '101_0',
'110_0', '111_1';
```

Composite types - records

- Like a struct in C

```
type iocell is record
buffer_inp: bit_vector(7 downto 0);
enable: bit;
buffer_out: bit_vector(7 downto 0);
end record;
```
- signal bussig1, bussig2: iocell;
- bussig1.enable <= '0';
bussig2 <= bussig1;

Attributes

- provide information about entities, architectures, types and signals
 - several predefined value, signal and range attributes that are useful
- scalar type value attributes
 - 'left leftmost value, 'right rightmost value
 - 'high highest value, 'low lowest value
 - 'length # elts in the array
 - e.g. sig1'high
- signal attribute
 - 'event is true if signal has just occurred
- range attribute
 - gives a signal's range e.g. buffer_inp'range is 7 downto 0

Example: Shift Right

- signal x: std_logic_vector(7 downto 0);
- y <= x(0) & x(x'high downto 1);

Binary, Octal and Hex Specifiers

- Base specifiers can be used to describe the base of a string
 - B for binary
 - O for octal
 - X for hexadecimal
- e.g. a <= X'7A';

CEG 5010: Rapid System Prototyping Section 4: VHDL Combinatorial and Sequential Logic

Philip Leong

Combinatorial logic: Concurrent Statements

- Boolean equations can be used in concurrent and signal assignment statements
- ```
architecture archmux of mux is
begin
 x(3) <= (a(3) and not(s(1)) and
 not(s(0)))
 or (b(3) and not(s(1)) and s(0))
 or (c(3) and s(1) and not(s(0)))
 or (d(3) and s(1) and s(0));
 ...
 x(0) <= (a(0) and not(s(1)) and
 not(s(0)))
 or (b(0) and not(s(1)) and s(0))
 or (c(0) and s(1) and not(s(0)))
 or (d(0) and s(1) and s(0));
end archmux;
```
- e.g. 4 bit mux
- ```
library ieee;
use ieee.std_logic_1164.all;
entity mux is port(
  a, b, c, d: in std_logic_vector(3 downto 0);
  s: in std_logic_vector(1 downto 0);
  x: out std_logic_vector(3 downto 0));
end mux
```

Logical Operations

- Note that unlike C or other languages *logical operators in VHDL have no precedence!*
- You must use parentheses to group the operators

with-select-when

- with selection_sig select
signal_name <=
value a when sel_sig1,
value b when sel_sig2,
value c when sel_sig3,
value d when sel_sig4;
- architecture archmux of mux is
begin
with s select
x <= a when "00",
b when "01",
c when "10",
d when "11",
"--" when others;
end archmux;
- note if a is a std_logic_vector, there are a wide range of other values each elt can take (e.g. '-', 'Z', 'L', 'H' etc)

when-else

- `x <= a when (s = '00') else
b when (s = '01') else
c when (s = '00') else
d;`
- this is different from with-select-when since the condition need not be mutually exclusive
 - in case of conflicts, earlier conditions have higher priority
- E.g. `j <= w when a='1' else
x when b='1' else
y when c='1' else
z when d = '1' else
'0';`
- priority encoder

quiz

- A) what does the following do?
`tmp <= (a, b, c, d);
with tmp select`
- B) how about
`tmp <= (a, b, c, d);
with tmp select`
- `j <= w when '1000';
x when '0100';
y when '0010';
z when '0001';
'0' when others;`
- `j <= w when "1 ---";
x when "- 1 -";
y when "-- 1 -";
z when "--- 1";
'0' when others;`

Answer

- A)
`j <= (a and not(b) and not(c) and not(d) and w)
or (not(a) and b and not(c) and not(d) and x)
or ...`
- B)
- error
 - during simulation `j <= w` only if `a` is '1' and `b,c,d` are the value '1'. NOT when `b,c,d` are '1' for instance!
 - Synthesis needs to behave like simulation and '*' is not a value that `a,b,c,d` can ever take in synthesis
 - '*' is not really a don't care

when-else conditions

- with-select-when are like switch statements in C
- when-else are like if-else in C
 - more powerful since condition can be an expression
 - `a <= b when ((c = d) and (e < f)) else g;`

std_match

- to get around the problem of b)
- if `a = "1 --1"` then `--` is always false in synthesis
- if `(std_match(a, "1 --1"))` then
 - evaluates true if `a(3)` and `a(0)` are equal to 1

Component instantiation

- VHDL does not define that certain components must be in the system
 - instantiation is system dependent
 - this makes it non-portable
 - however it would be optimized for the architecture

Sequential statements

- Sequential statements are those contained in a process, function or procedure
- Order of signals affects how the logic is synthesized
- **Sequential statements can create combinatorial logic**
- Following are equivalent

```
similar1: process(addr)
begin
  step <= '0';
  if (addr > x'0F') then
    step <= '1';
  end if;
end process;

similar2: process(addr)
begin
  if (addr > x'0F') then
    step <= '1';
  else
    step <= '0';
  end if;
end process;
```

Implied memory

```
notsimilar: process(addr)
begin
  if (addr > x'0F') then
    step <= '1';
  end if;
end process;
```

- no initial values in VHDL
- this will cause step to become '1' and stay there forever when addr > x'0F'
 - what circuit can do this? (hint must have memory)

if-then-elsif

```
if (cond1) then
  action1;
elsif (cond2) then
  action2;
else
  action3;
```

- What logic statement does this generate?
- How is this related to when-else?
- Which is more powerful?

case-when

```
process(addr)
begin
  case addr is
    when '001' => decode <= X'11';
    when '111' => decode <= X'11';
    when '011' => decode <= X'11';
    when others => decode <= X'00';
  end case;
end process;
```

- Similar to when-else but can change the output expression

Synchronous logic - a D flip flop

```
library ieee;
use ieee.std_logic_1164.all;
entity
  dff_logic is port (d, clk: in std_logic; q:
    out std_logic);
end dff_logic;
architecture example of dff_logic is
begin
  process (clk) begin
    if (clk'event and clk = '1') then
      q <= d;
    end if;
  end process;
end example;
```

- Only clk is in sensitivity list
 - changes in d should not run the process (many will anyway)
- if (clk'event and clk = '1')
 - standard way to recognize a rising edge
 - how do we do a falling edge?
- How about a level sensitive latch?
- A T flip flop?

Bad VHDL code

```
• Putting and else after an if (clk'event and clk='1') is not clear don't use it since it may not be portable
if (clk'event and clk = '1') then
  q <= d;
else
  q <= a;
end if;
```

Wait statements and rising_edge

- Instead of using a process with a sensitivity list and 'event can use
- Can also use rising_edge or falling_edge

```
architecture example2 of dff_logic
is
begin
process begin
wait until (clk = '1');
q <= d;
end process;
end example2;

process (clk)
begin
if rising_edge(clk) then
q <= d;
end if;
end process;
```

Asynchronous reset

- How do we do a *synchronous* reset?

```
process (clk, reset)
begin
if (reset = '1') then
q <= '0';
elsif (clk'event and clk = '1') then
q <= d;
end if;
end process;
```

An 8 bit counter with preload of 5

```
entity cnt8 is port(
txclk, grst: in std_logic;
enable, load: in std_logic;
data: in std_logic_vector(7 downto 0);
cnt: buffer
std_logic_vector(7 downto 0));
end cnt8;

architecture archcnt8 of cnt8 is
begin
count: process(grst, txclk)
begin
if (grst = '1') then
cnt <= '0000101';
elsif (txclk'event and txclk = '1') then
if (load = '1') then
cnt <= data;
elsif (enable = '1') then
cnt <= cnt + 1;
end if;
end if;
end process count;
end archcnt8;
```

Aggregates

- cnt <= (others => '0'); -- all elements of cnt set to 0
- cnt <= ('1', '0', others => '1'); -- cnt becomes "10" & all 1's dep on cnt's size
- cnt <= (others => 'Z') -- high impedance output
- cnt <= data(7) & data -- & is the concatenation operator

Tristate and Bidirectional signals

- How do we make the counter have a tristate output?
- How about using the same bus for output and loading?

Tristate and Bidirectional signals

- Tristate
 - cnt_out: buffer std_logic_vector(7 downto 0);
 - cnt_out <= (others => 'Z') when oe = '0' else cnt;
- Bidirectional
 - cnt_out: inout std_logic_vector(7 downto 0);
 - if (load = '1') then
cnt <= cnt_out;
elsif (enable = '1') then
cnt <= cnt + 1;
end if;
 - cnt_out <= (others => 'Z') when oe = '0' else cnt;

For loops

- Variables automatically declared in a loop
 - for i in 7 downto 0 loop
data(i) <= '0';
end loop;
- Next is like continue in C
 - for i in 7 downto 0 loop
if i = 4 then
next;
else
data(i) <= '0';
end loop;

While loops

- Variables not needed often in synthesis
 - an exception is loop counters

```
reg_array: process (rst, clk)
  variable i: integer := 0; -- note := not <= for variables
begin
  while i < 7 loop
    data(i) := 0;
    i := i + 1;
  end loop;
end process;
```