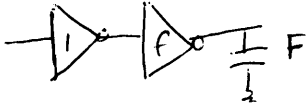
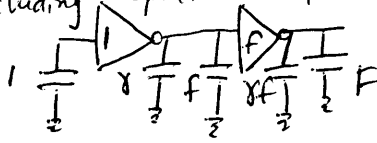


Transistor sizing for min energy

For  recall $t_p = t_{po} \left(\left(1 + \frac{f}{\gamma}\right) + \left(1 + \frac{F}{\gamma f}\right) \right)$, $t_{po} \propto \frac{V_{DD}}{V_{DD} - V_{TE}}$
 where $V_{TE} = V_T + V_{DSAT}/2$ and $C_{int} = \gamma C_{gin}$

Also including capacitance of buffers

 $E = V_{DD}^2 C_{gin} \left((1 + \gamma)(1 + f) + F \right)$


Reference Implementation $V_{DD} = V_{ref}$, $\gamma = 1$, $f = 1$

$$t_{pref} = t_{poref} (3 + F) \quad t_{poref} \propto \frac{V_{ref}}{V_{ref} - V_{TE}}$$

$$E_{ref} = V_{ref}^2 C_{gin} (4 + F)$$

Trick: by varying V_{DD} & f , we can change t_p and E .


Suppose we want

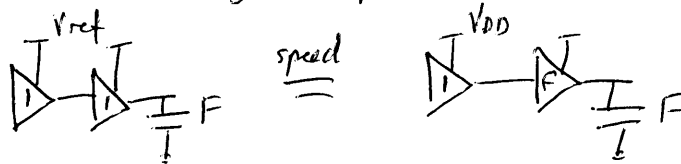

$$\frac{t_p}{t_{pref}} = 1 \Rightarrow \frac{t_{po} (2 + f + F/f)}{t_{poref} (3 + F)} = 1$$

$$\Rightarrow \frac{V_{DD}}{V_{ref}} \frac{V_{ref} - V_{TE}}{V_{DD} - V_{TE}} \frac{(2 + f + F/f)}{3 + F} = 1$$

Suppose we want

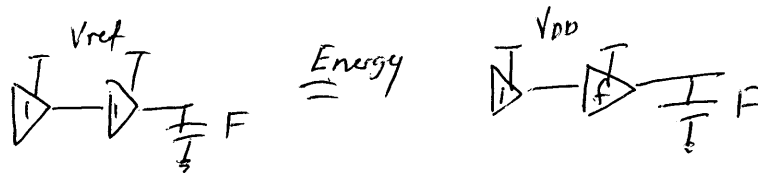

$$\frac{E}{E_{ref}} = 1 \Rightarrow \frac{V_{DD}^2}{V_{ref}^2} \left(\frac{2 + 2f + F}{4 + F} \right) = 1$$

TRANSISTOR DRAIN CURRENT SPREADSHEET

VDD 2.5 V

NMOS Parameters

VT0	0.43 Volts	VT0	-0.4 Volts
GAMMA	0.4 V ⁿ 0.5	GAMMA	-0.4 V ⁿ 0.5
VDSAT	0.63 V	VDSAT	-1 V
k'	115 uANV ²	k'	-30 uANV ²
LAMBDA	0.05 V ⁿ -1	LAMBDA	-0.1 V ⁿ -1
PHIF	0.45 V	PHIF	0.3 V

PMOS Parameters

VT	0.43	VT	-0.4
VGT	2.07 V	VGT	-2.1 V
Vmin	0.63 V	Vmin	-1 V
W/L	1	W/L	1
k'W/L	115 uANV ²	k'W/L	-30 uANV ²

ID(no lambda)	127.14975 uA	ID(no lambda)	-48 uA
ID (w lambda)	143.0434688 uA	ID (w lambda)	-60 uA
IDSAT	127.14975 uA	IDSAT	-48 uA

W	0.25 um	BETA (Wp/Wn)	1
L	0.25 um	W	0.25 um
VGS	2.5 V	L	0.25 um
VDS	2.5 V	VGS	-2.5 V
VSB	0 V	VDS	-2.5 V
		VSB	0 V

ID	143.0434688 uA	VELSAT	
Req	13312.7146 ohms	ID	-60 uA
		Req	31467.0139 ohms
		VELSAT	