

Hardware Compilation

Slides courtesy of Prof Wayne Luk
Imperial College London

wl 2008 1

Hardware compilation

- computers are slow, bulky, consume much power
 - machine code interpreters
 - get rid of fetch/decode stage? ↓CPI? ↓clock delay?
- compile programs directly into hardware
 - hardware is parallel, hence fast
 - distributed control: no program counter
 - variables → registers, expressions → combinational circuit
 - applications: multimedia, communication, robotics
 - but hardware is inflexible?

wl 2008 2

Field-Programmable Gate Array (FPGA)

- a matrix of programmable elements, including: logic blocks, storage elements, interconnections
- 100K to 10000K gates: system-on-a-chip, can include multipliers, instruction processors e.g. ARM
- clock speed up to 1000MHz (50-200MHz common)
- some can be reprogrammed within milliseconds (even partially reprogrammable)
- off-the-shelf parts, see www.altera.com, www.xilinx.com approaching speed of hardware, flexibility of software
- stand-alone or used with microprocessor

wl 2008 3

Occam and Handel-C

- based on CSP notation; commercial version: Handel-C
- primitive processes:

skip stop $v := e$ $c ! e$ $c ? e$ delay

↑ var ↑ expr ↑ chan output ↑ chan input
- composite processes:

SEQ P Q PAR P Q IF B P WHILE B P
ALT B_i P_i (conditional on input ready in B_i)
- channel joins two processes at any time


one outputs $\left[\begin{matrix} \text{CHAN } C: \\ \text{PAR} \\ C ! E \\ C ? X \end{matrix} \right] = \left[X := E \right]$ the other inputs

} not examined
- produce data processors and instruction processors
- can also compile declarative programs into hardware

wl 2008 4

Expression and variable

 - expression: implemented using combinational hardware
 - no combinational loops
 - ensure propagation delay shorter than clock period (usually)
- variable: implemented using D type flip-flop and a multiplexor (mux)
 - mux allows conditional update of D type flip-flop (when CE = 1)



w1 2008 5


Control strategy

- use a single-cycle pulse (the token) to activate a control circuit (e.g. assignment)
- environment supplies a token to start (s), the token reappears at finish (f) when the statement completes execution
- control assumption: a control circuit does not create or destroy a token, provided that the environment does not offer a second token before the first token reappears
- the assignment circuit can accept token every cycle

w1 2008 6

Assignment statement $v := exp$

 - provide control circuit to signal assignment, statement is completed after n cycles
- n depends on propagation delay of exp, usually n=1




- concurrent assignment: $v0, v1 := exp0, exp1$
use the same control circuit for the CE inputs for $v0, v1$ hardware

w1 2008 7


Assignment: general case

 - need multiplexing to support assigning different values to a variable at different times
e.g. $V := exp0; \dots ; V := exp1$



w1 2008 8

Initialisation

 

- provides the initial token to get system going
- assumes D-latch initialised to zero

w1 2008 9

Skip, delay and stop


- skip: does nothing, terminates immediately



- delay: does nothing, terminates after 1 cycle




 - stop: never terminates perhaps raise an alarm



w1 2008 10



Sequential composition

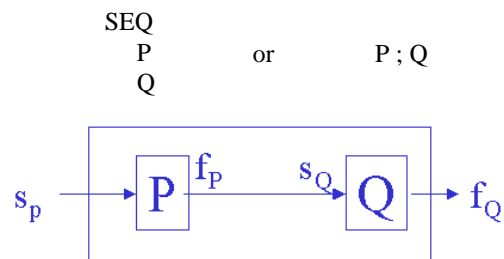

- if P, Q satisfy the control assumption, then P;Q satisfies the control assumption
- only control signals are shown in the diagram

w1 2008 11

Conditional

  


- either P or Q (not both) should get the token

w1 2008 12

Iteration


WHILE E P or while (E) P

 

- what happens with the program while (1) skip?

w1 2008 13

Example: simple data processor

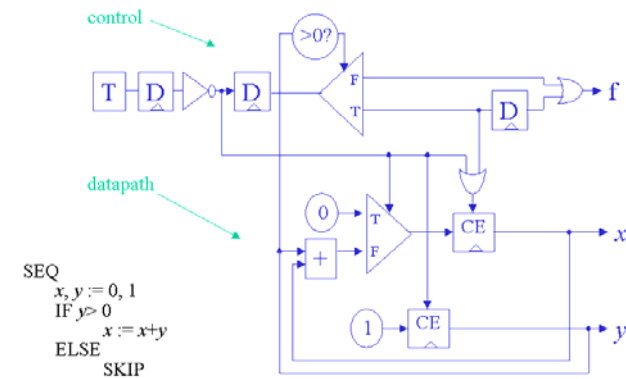


w1 2008 14

The par construct

- adding to parallelism in expression evaluation and concurrent assignment
- can run program components in parallel if:
 - no variables in common, operating independently
 - communicate with each other via channels
 - share variables with each other, with restrictions
- replicate tokens, one for each parallel component
- terminates when all program fragments have terminated
- control circuit should have no time overhead:
 - start parallel execution immediately
 - terminate immediately when appropriate

w1 2008 15

Control circuit for par

 

- SR flip-flop: once set, remains set until R input high
- or-gate: allows immediate termination
- implementation and optimisation possible


w1 2008 16

Example: Fibonacci program

- int_7 R1, R2 } variable declaration
SEQ (generate data registers)
- R1, R2 := 0, 1 } init. } generate control
- WHILE TRUE } compute } hardware, datapath
- R1, R2 := R2, R1+R2 } next fib. }
- time= 0 R1 = 0 R2 = 1
- 1 1 1
- 2 1 2
- 3 2 3
- 4 3 5
- 5 5 8

w1 2008 17

Fibonacci data processor

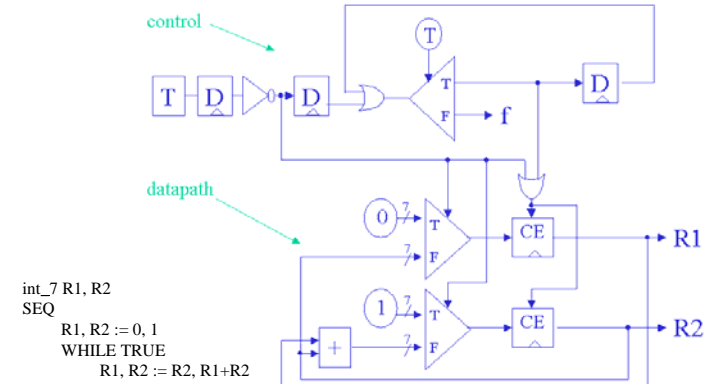

w1 2008 18

Compiling instruction processors

- define instruction set, possibly application dependent
- develop interpreter for instruction, e.g.
 - variable declaration (e.g. PC, IR)
 - WHILE TRUE
 - SEQ
 - fetch_next_instruction
 - decode_and_execute
 } generic format
- convert application programs into machine code; compile instruction interpreter into hardware
- facilitate customisation of resources to application
 - remove resources for unused instructions
 - combine groups of instructions into a new instruction

w1 2008 19

Fibonacci instruction processor

- 7 instructions
 - int_4 PC: int_7 IR, A: [16] int_7 M:
 - IR take 4
 - IR drop 4
 - operand(IR) 4-bit register
 - opcode(IR) 7-bit register
 - MSB
 - WHILE TRUE
 - SEQ
 - PC, IR := PC + 1, M[PC] ← fetch
 - CASE (opcode (IR)) ← decode, exec.
 - 0: SKIP ← SKIP instr.
 - 1: A := operand(IR) -- load const ← LDC instr.
 - 2: A := M[operand(IR)] -- load accum ← LDA instr.
 - 3: M[operand(IR)] := A -- store accum ← STA instr.
 - 4: A := A + M[operand(IR)] ← ADDA instr.
 - 5: PC := operand(IR) ← JMP instr.
 - 6: IF A < 0 THEN PC := operand(IR) ← JLT instr.
- array of 16 7-bit registers, initialised with user program

w1 2008 20

Fibonacci machine code

address	M[address]	behaviour	high-level behaviour
0	LDC 0	A := 0	R1 := 0
1	STA R1	R1 := A	
2	LDC 1	A := 1	R2 := 1
3	STA R2	R2 := A	
4	ADDA R1	A := A + R1	x := R1+R2
5	STA x	x := A	
6	LDA R2	A := R2	R1 := R2
7	STA R1	R1 := A	
8	LDA x	A := x	R2 := x (with R2 := A at address 3)
9	JMP 3	goto 3	
13	VAR R1		
14	VAR R2		
15	VAR x		

loop contains 7 instructions,
2 cycles per instruction

w1 2008 21

Variations of instruction processors

- example: repeatedly calculate $x^2 + y^2$
- possible implementations:
 - (a) only **add** instruction, square by repeated add, accumulator style
 - (b) only **add** instruction, square by repeated add, load-store style
 - (c) **add** and **square** instructions, accumulator style
 - (d) **add** and **square** instructions, load-store style
 - (e) custom **sumsq** instruction: dedicated circuit for $x^2 + y^2$
 - (f) pipelined version of above: overlap fetch/decode/execute
- size / performance trade-offs
 - (d) largest, fastest: 938 gates/registers, 14 cycles
 - (e) smallest, slowest: 500 gates/registers, 81 cycles

w1 2008 22

Reconfiguration: virtual hardware

- exploit reconfigurability
 - not all operations are active all the time
 - download new operations while in service
 - reduce size, reduce power consumption, increase flexibility
- applications
 - different data formats/standards, future proof
 - adapt to environment, e.g. error correction based on noise level
 - partition large *virtual* hardware for small physical device
- reduce reconfiguration time: partially reconfigure devices and systems
 - minimise reconfigurable parts, maximise re-use
 - morphing: overlap reconfiguration and operation
 - store ready-made configurations, or synthesis at run time

w1 2008 23

Summary

- hardware compilation
 - program directly to hardware; token-passing control
 - data processor: avoid instruction fetch/decode, specialise ALU
 - exploit parallelism, pipelining, locality
 - target latest FPGA: 10M programmable gates/connections
- compilation strategy for parallel imperative language
 - variables → registers, expressions → combinational circuit
 - control circuit: token to activate corresponding datapath
- Further reading
 - Page and Luk: Compiling occam into FPGAs, Proc. FPL'91
 - Countinho, Jiang and Luk: Interleaving behavioral and cycle-accurate descriptions for reconfigurable hardware compilation, Proc. FCCM'05
 - Styles and Luk: Exploiting program branch probabilities in hardware compilation, IEEE Trans. on Computers, Nov. 04

w1 2008 24